

# AMERICAN INTERNATIONAL UNIVERSITY-BANGLADESH

408/1, Kuratoli, Khilkhet, Dhaka 1229, Bangladesh



**Assignment Title:** Verification of Kirchoff's Voltage Law (KVL) and Kirchoff's Current Law (KCL).

**Assignment No:** 02

**Date of Submission:** October 16, 2022

**Course Title:** Introduction to Electrical Circuits Laboratory

**Course Code:** COE2102

**Section:** T

**Semester:** FALL

2022-23

**Course Teacher:** BISHWAJIT BANIK PATHIK

**Declaration and Statement of Authorship:**

1. I/we hold a copy of this Assignment/Case-Study, which can be produced if the original is lost/damaged.
2. This Assignment/Case-Study is my/our original work and no part of it has been copied from any other student's work or from any other source except where acknowledgement is made.
3. No part of this Assignment/Case-Study has been written for me/us by any other person except where such collaboration has been authorized by the concerned teacher and is clearly acknowledged in the assignment.
4. I/we have not previously submitted or currently submitting this work for any other course/unit.
5. This work may be reproduced, communicated, compared and archived for the purpose of detecting plagiarism.
6. I/we give permission for a copy of my/our marked work to be retained by the Faculty for review and comparison, including review by external examiners.
7. I/we understand that Plagiarism is the presentation of the work, idea or creation of another person as though it is your own. It is a form of cheating and is a very serious academic offence that may lead to expulsion from the University. Plagiarized material can be drawn from, and presented in, written, graphic and visual form, including electronic data, and oral presentations. Plagiarism occurs when the origin of them arterial used is not appropriately cited.
8. I/we also understand that enabling plagiarism is the act of assisting or allowing another person to plagiarize or to copy my/our work.

\* Student(s) must complete all details except the faculty use part.

\*\* Please submit all assignments to your course teacher or the office of the concerned teacher.

**Group Name/No.:** 8 / Ground

No	Name	ID	Program	Signature
1	MD. SHOHANUR RAHMAN SHOHAN	22-46013-1	B. Sc. in CSE	Shohan
2	MAHNNAZ TABASSUM ORPITA	22-46024-1	B. Sc. in CSE	Orpita
3	LIDA KHAN MUKTI	22-47000-1	B. Sc. in CSE	Lida
4	TARIN SULTANA	22-47045-1	B. Sc. in CSE	Tarin
5	A. F. M. RAFIUL HASSAN	22-47048-1	B. Sc. in CSE	Rafiul

**Faculty use only**

FACULTY COMMENTS

Marks Obtained

Total Marks

G

## Abstract:

The experiment was conducted to investigate the verification of Kirchoff's Voltage Law (KVL) and Kirchoff's Current Law (KCL). There are two sections in this experiment. In the first circuit Kirchoff's Voltage Law (KVL) will be verified and in the second Kirchoff's Current Law (KCL) will be verified. Some basic tools like resistor, connecting wire, trainer board, AVO meter or multimeter, DC source etc are used in this experiment. By completing this experiment, we were able to develop an understanding of Kirchoff's Voltage Law (KVL) and Kirchoff's Current Law (KCL) practically. And, finally measured values are going to be verified with calculated values.

## Theory:

Kirchoff's voltage law (KVL):

Kirchoff's voltage law (KVL) in a DC circuit

state that, "the algebraic sum of the voltage drop around any closed path is equal to the algebraic sum of the voltage rises". In other words, "the algebraic sum of the voltage rises and drops around any closed path is equal to zero". A plus (+) sign is assigned for the potential rises (-to+) and minus sign (-) is assigned to a potential drop (+to-). In symbolic form, Kirchoff's Voltage Law (KVL) can be expressed as,

$\sum_c V = 0$ , where C is used for closed loop and V is used for the potential rises and drops.

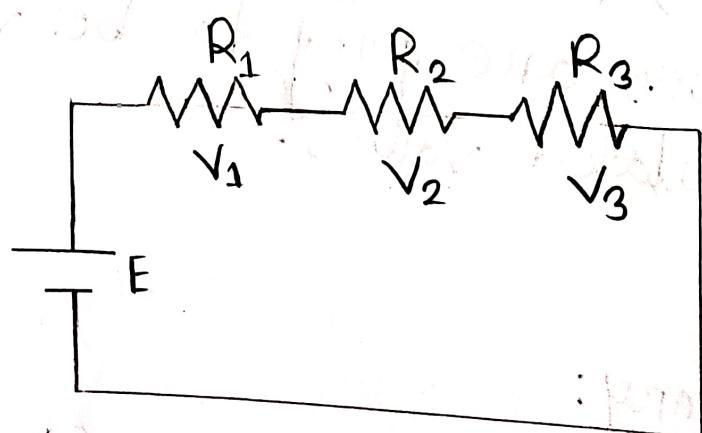


Figure - 1

## Analysis of KVL circuit:

For doing a complete analysis of KVL, with the given values of circuit parameters follow the following steps: step 1: calculate the value of supply current:  $I = \frac{E}{(R_1 + R_2 + R_3)}$

step 2: calculate  $V_1$ ,  $V_2$  and  $V_3$ :

$$V_1 = I \times R_1 \quad V_2 = I \times R_2 \quad V_3 = I \times R_3$$

step 3: Use KVL to verify:

$$\sum_c V = 0 \quad \text{or} \quad E - V_1 - V_2 - V_3 = 0$$

## Kirchhoff's Current Law (KCL):

Kirchhoff's Current Law (KCL) in a DC circuit states that, "the algebraic sum of the currents entering and leaving an area, system or junction is zero". In other words, "the sum of the currents entering an area, system or junction must be equal the sum of the currents leaving"

the area, system or junction". In equation form,  $\sum I_{\text{Entering}} = \sum I_{\text{Leaving}}$

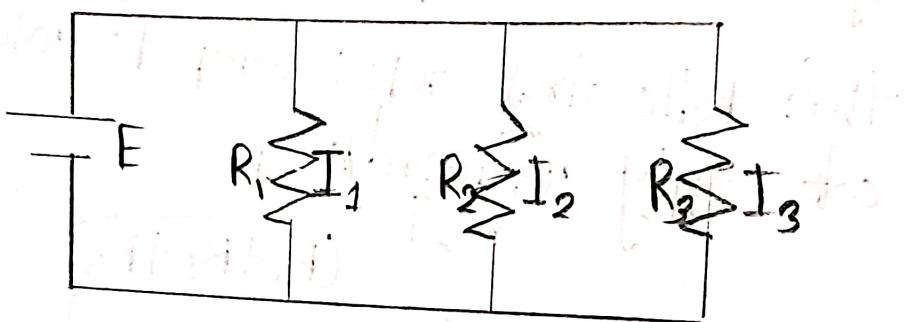


Figure - 2

Analysis of KCL circuit:

for doing a complete analysis of KCL, with the given values of circuit parameters follow the following steps:

step 1: calculate the value of equivalent resistance of circuit:

$$R_{\text{eq}} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

step 2: calculate supply current I:

$$I = \frac{E}{R_{\text{eq}}}$$

step 3: calculate current through different branches:

$$I_1 = \frac{E}{R_1} \quad I_2 = \frac{E}{R_2} \quad I_3 = \frac{E}{R_3}$$

step 4: use KCL to verify:

$$\sum I \text{ Entering} = \sum I \text{ Leaving} \quad \text{or } I = I_1 + I_2 + I_3$$

List of Equipment:

1. Resistors

2. Connecting wires

3. Trainer Board

4. AVO meter or multimeter

5. DC source.

Circuit  
Diagram

precautions:

1. The circuit was connected so carefully

2. The entire connection diagram

was checked before connecting

the supply to the circuit.

## Experimental procedure:

for KVL: The circuit was connected as shown in the figure-1. The voltage was measured across each elements of the circuit. The following table was filled with necessary calculations.

table-1

No of Obs.	$R_1$ $K\Omega$	$R_2$ $K\Omega$	$R_3$ $K\Omega$	$V$	$V_1$		$V_2$		$V_3$		$V = V_1 + V_2 + V_3$		% Error = $\frac{V_{cal} - V_{exp}}{V_{exp}} \times 100$	
					C	M	C	M	C	M	C	M		
1	2.2	4.6	3.3	5	4.97	1.089	1.08	2.277	2.30	1.633	1.63	5	5.01	0.2
2	2.2	4.6	3.3	8	8.01	1.742	1.72	3.643	3.69	2.613	2.61	8	8.01	0.25
3	2.2	4.6	3.3	10	9.95	2.178	2.16	4.556	4.61	3.267	3.27	10	9.95	0.4
4	2.2	4.6	3.3	12	11.96	2.613	2.59	5.465	5.54	3.920	3.92	12	11.96	0.41
5	2.2	4.6	3.3	15	15.02	3.267	3.22	6.831	6.90	4.900	4.89	15	15.01	0.06

for KCL: The circuit was connected as shown in the figure-1. The current across each branches of the circuit was measured. The following table was filled with necessary calculations.

Table - 2

No of Obs.	$R_1$ K $\Omega$	$R_2$ K $\Omega$	$R_3$ K $\Omega$	I	$I_1$		$I_2$		$I_3$		$I = I_1 + I_2 + I_3$		$\% \text{ Error} = \frac{\%(\text{mV}-\text{cV})}{\text{cV}}$	
					C	M	C	M	C	M	C	M		
1	2.2	4.6	3.3	0.004878	0.0048	0.00252	0.0023	0.001086	0.0011	0.001515	0.0015	0.004878	0.0049	0.45
2	2.2	4.6	3.3	0.001804	0.0019	0.00363	0.0037	0.001739	0.0017	0.002424	0.0025	0.001804	0.0019	1.23
3	2.2	4.6	3.3	0.009756	0.0098	0.004545	0.0046	0.002173	0.0022	0.009303	0.003	0.009756	0.0098	0.45
4	2.2	4.6	3.3	0.0011707	0.0011	0.005454	0.0055	0.002608	0.0026	0.003636	0.0036	0.0011707	0.00117	0.05
5	2.2	4.6	3.3	0.004634	0.0047	0.006818	0.0069	0.003260	0.0032	0.004545	0.0046	0.004634	0.0047	0.45

## Results and calculations:

for KVL:

$$R_1 = 2.2 \text{ k}\Omega = 2.2 \times 10^3 \Omega$$

$$R_2 = 4.6 \text{ k}\Omega = 4.6 \times 10^3 \Omega$$

$$R_3 = 3.3 \text{ k}\Omega = 3.3 \times 10^3 \Omega$$

$$\begin{aligned} R &= R_1 + R_2 + R_3 = (2.2 + 4.6 + 3.3) \\ &= 10.1 \text{ k}\Omega \\ &= 10.1 \times 10^3 \Omega \end{aligned}$$

Observation No: 1

$$V = 5V$$

$$I = \frac{V}{R} = \frac{5}{10.1 \times 10^3} = 0.495 \times 10^{-3} A$$

calculated value:

$$V = 5V$$

$$\text{and } V_1 + V_2 + V_3 = 1.089 + 2.277 + 1.633 \\ = 5V$$

measured value:

$$V = 4.97$$

$$\text{and } V_1 + V_2 + V_3 = 1.08 + 2.30 + 1.63 \\ = 5.01V$$

$$\% \text{ Error} = \frac{5.01 - 5}{5} \times 100 \\ = 0.2\%$$

## Observation No : 2

$$V = 8V$$

$$I = \frac{V}{R} = \frac{8}{10.1 \times 10^3} = 0.792 \times 10^{-3} A$$

$$V_1 = IR_1 = 0.792 \times 10^{-3} \times 2.2 \times 10^3 = 1.742V$$

$$V_2 = IR_2 = 0.792 \times 10^{-3} \times 4.6 \times 10^3 = 3.643V$$

$$V_3 = IR_3 = 0.792 \times 10^{-3} \times 3.3 \times 10^3 = 2.613V$$

Calculated value:

$$V = 8V$$

$$\text{and } V_1 + V_2 + V_3 = 1.742 + 3.643 + 2.613 = 8V$$

Measured value:

$$V = 8V$$

$$\text{and } V_1 + V_2 + V_3 = 1.72 + 3.69 + 2.61 = 8.02V$$

$$\% \text{ Error} = \frac{8.02 - 8}{8} \times 100 = 0.25\%$$

Observation No : 3

$$V = 10V$$

$$I = \frac{V}{R} = \frac{10}{10.1 \times 10^3} = 0.99 \times 10^{-3} A$$

$$V_1 = IR_1 = 0.99 \times 10^{-3} \times 2.2 \times 10^3 = 2.178V$$

$$V_2 = IR_2 = 0.99 \times 10^{-3} \times 4.6 \times 10^3 = 4.554V$$

$$V_3 = IR_3 = 0.99 \times 10^{-3} \times 3.3 \times 10^3 = 3.267V$$

calculated value:

$$V = 10V$$

$$\text{and } V_1 + V_2 + V_3 = 2.178 + 4.554 + 3.267 = 10V$$

Measured value:

$$V = 10.04$$

$$\text{and } V_1 + V_2 + V_3 = 2.16 + 4.61 + 3.27 = 10.04$$

$$\% \text{ Error} = \frac{10.04 - 10}{10} \times 100 = 0.4\%$$

Observation No: 4

$$V = 12V$$

$$I = \frac{V}{R} = \frac{12}{10.1 \times 10^3} = 1.188 \times 10^{-3} A$$

$$V_1 = IR_1 = 1.188 \times 10^{-3} \times 2.2 \times 10^3 = 2.613V$$

$$V_2 = IR_2 = 1.188 \times 10^{-3} \times 4.6 \times 10^3 = 5.464V$$

$$V_3 = IR_3 = 1.188 \times 10^{-3} \times 3.3 \times 10^3 = 3.920V$$

Calculated value:

$$V = 12V$$

$$\text{and } V_1 + V_2 + V_3 = 2.613 + 5.465 + 3.920 = 12V$$

Measured value:

$$V = 11.06$$

$$\text{and } V_1 + V_2 + V_3 = 2.59 + 5.54 + 3.92 = 12.05V$$

$$\% \text{ Error} = \frac{12.05 - 12}{12} \times 100 \\ = 0.41\%$$

## Observation NO: 5

$$V = 15V$$

$$I = \frac{V}{R} = \frac{15}{10.1 \times 10^3} = 1.485 \times 10^{-3} A$$

$$V_1 = IR_1 = 1.485 \times 10^{-3} \times 2.2 \times 10^3 = 3.267 V$$

$$V_2 = IR_2 = 1.485 \times 10^{-3} \times 4.6 \times 10^3 = 6.831 V$$

$$V_3 = IR_3 = 1.485 \times 10^{-3} \times 3.3 \times 10^3 = 4.900 V$$

calculated value:

$$V = 15V$$

$$\text{and } V_1 + V_2 + V_3 = 3.267 + 6.831 + 4.900 = 15V$$

Measured value:

$$V = 15.02$$

$$\text{and } V_1 + V_2 + V_3 = 3.22 + 6.90 + 4.89 = 15.01 V$$

$$\% \text{ Error} = \frac{15.01 - 15}{15} \times 100 = 0.06\%$$

$$\text{For KCL: } R_1 = 2.2 \text{ k}\Omega = 2.2 \times 10^3 \Omega$$

$$R_2 = 4.6 \text{ k}\Omega = 4.6 \times 10^3 \Omega$$

$$R_3 = 3.3 \text{ k}\Omega = 3.3 \times 10^3 \Omega$$

$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

$$R_{eq} = \left( \frac{1}{2.2} + \frac{1}{4.6} + \frac{1}{3.3} \right)^{-1}$$

$$= 1.025 \text{ k}\Omega = 1.025 \times 10^3 \Omega$$

servation No: 1

Resultant resistance = 10

$$V = 5V$$
$$I = \frac{V}{R_{eq}} = \frac{5}{1.025 \times 10^3} = 4.878 \times 10^{-3} A$$

$$I_1 = \frac{V}{R_1} = \frac{5}{2.2 \times 10^3} = 2.252 \times 10^{-3} A$$

$$I_2 = \frac{V}{R_2} = \frac{5}{4.6 \times 10^3} = 1.086 \times 10^{-3} A$$

$$I_3 = \frac{V}{R_3} = \frac{5}{3.3 \times 10^3} = 1.515 \times 10^{-3} A$$

Calculated value:

$$I = 4.878 \times 10^{-3} A$$

$$\text{and } I_1 + I_2 + I_3 = (2.252 \times 10^{-3}) + (1.086 \times 10^{-3}) \\ + (1.515 \times 10^{-3}) = 4.878 \times 10^{-3} A$$

Measured value:

$$I = 4.878 \times 10^{-3} A$$

$$\text{and } I_1 + I_2 + I_3 = (2.3 \times 10^{-3}) + (1.1 \times 10^{-3}) \\ + (1.5 \times 10^{-3}) = 4.9 \times 10^{-3} A$$

$$\% \text{ Error} = \frac{(4.9 - 4.878) \times 10^{-3}}{4.878 \times 10^{-3}} \times 100$$

$$= 0.45 \%$$

## Observation NO: 2

$$V = 8V$$

$$I = \frac{V}{R_{eq}} = \frac{8}{1.025 \times 10^3} = 7.804 \times 10^{-3} A$$

$$I_1 = \frac{V}{R_1} = \frac{8}{2.2 \times 10^3} = 3.636 \times 10^{-3} A$$

$$I_2 = \frac{V}{R_2} = \frac{8}{4.6 \times 10^3} = 1.739 \times 10^{-3} A$$

$$I_3 = \frac{V}{R_3} = \frac{8}{3.3 \times 10^3} = 2.424 \times 10^{-3} A$$

calculated value:

$$I = 7.804 \times 10^{-3} A$$

$$\text{and } I_1 + I_2 + I_3 = (3.636 \times 10^{-3}) + (1.739 \times 10^{-3}) \\ + (2.424 \times 10^{-3}) = 7.804 \times 10^{-3} A$$

Measured value:

$$I = 7.9 \times 10^{-3} A$$

$$\text{and } I_1 + I_2 + I_3 = (3.7 \times 10^{-3}) + (1.7 \times 10^{-3}) \\ + (2.5 \times 10^{-3}) = 7.9 \times 10^{-3} A$$

$$\% \text{ Error} = \frac{(7.9 - 7.804) \times 10^{-3}}{7.804 \times 10^{-3}} \times 100 = 1.23\%$$

## Observation No:- 3

$$V = 10V$$

$$I = \frac{V}{R_{eq}} = \frac{10}{1.025 \times 10^3} = 9.756 \times 10^{-3} A$$

$$I_1 = \frac{V}{R_1} = \frac{10}{2.2 \times 10^3} = 4.545 \times 10^{-3} A$$

$$I_2 = \frac{V}{R_2} = \frac{10}{4.6 \times 10^3} = 2.173 \times 10^{-3} A$$

$$I_3 = \frac{V}{R_3} = \frac{10}{3.3 \times 10^3} = 3.030 \times 10^{-3} A$$

calculated value:

$$I = 0.756 \times 10^{-3} A$$

$$\text{and } I_1 + I_2 + I_3 = (4.545 \times 10^{-3}) + (2.173 \times 10^{-3}) + (3.030 \times 10^{-3}) = 0.756 \times 10^{-3} A$$

Measured value:

$$I = 0.8 \times 10^{-3} A$$

$$\text{and } I_1 + I_2 + I_3 = (4.6 \times 10^{-3}) + (2.2 \times 10^{-3}) + (3.0 \times 10^{-3}) = 0.8 \times 10^{-3} A$$

$$\% \text{ Error} = \frac{(0.8 - 0.756) \times 10^{-3}}{0.756 \times 10^{-3}} \times 100 = 0.45\%$$

Observation No: 4:

$$V = 12 V$$

$$I = \frac{V}{R_{eq}} = \frac{12}{1.025 \times 10^3} = 11.707 \times 10^{-3} A$$

$$I_1 = \frac{V}{R_1} = \frac{12}{2.2 \times 10^3} = 5.454 \times 10^{-3} A$$

$$I_2 = \frac{V}{R_2} = \frac{12}{4.6 \times 10^3} = 2.608 \times 10^{-3} A$$

$$I_3 = \frac{V}{R_3} = \frac{12}{3.3 \times 10^3} = 3.636 \times 10^{-3} A$$

Calculated value:

$$I = 11.707 \times 10^{-3} A$$

$$\text{and } I_1 + I_2 + I_3 = (5.454 \times 10^{-3}) + (2.608 \times 10^{-3}) + (3.636 \times 10^{-3}) = 11.707 \times 10^{-3} A$$

Measured value:

$$I = 11.7 \times 10^{-3} A$$

$$\text{and } I_1 + I_2 + I_3 = (5.5 \times 10^{-3}) + (2.6 \times 10^{-3}) + (3.6 \times 10^{-3}) = 11.7 \times 10^{-3} A$$

$$\% \text{ Error}_1 = \frac{(11.7 - 11.707) \times 10^{-3}}{11.707 \times 10^{-3}} \times 100 = 0.05\%$$

Observation No: 5

$$V = 15 V$$

$$I = \frac{V}{R_{eq}} = \frac{15}{1.025 \times 10^3} = 14.634 \times 10^{-3} A$$

$$I_1 = \frac{V}{R_1} = \frac{15}{2.2 \times 10^3} = 6.818 \times 10^{-3} A$$

$$I_2 = \frac{V}{R_2} = \frac{15}{4.6 \times 10^3} = 3.260 \times 10^{-3} A$$

$$I_3 = \frac{V}{R_3} = \frac{15}{3.3 \times 10^3} = 4.545 \times 10^{-3} A$$

Calculated value:

$$I = 14.634 \times 10^{-3} A$$

$$\text{and } I_1 + I_2 + I_3 = (6.818 \times 10^{-3}) + (3.260 \times 10^{-3}) + (4.545 \times 10^{-3}) = 14.634 \times 10^{-3} A$$

Measured value:

$$I = 14.7 \times 10^{-3} A$$

$$\text{and } I_1 + I_2 + I_3 = (6.9 \times 10^{-3}) + (3.2 \times 10^{-3}) + (4.6 \times 10^{-3}) = 14.7 \times 10^{-3} A$$

$$\% \text{ Error}_1 = \frac{(14.7 - 14.634) \times 10^{-3}}{14.634 \times 10^{-3}} \times 100 \\ = 0.45\%$$

## Discussion:

1. The trainer board and multimeter were checked before the start of the experiment.
2. Both calculated and measured value were taken carefully.
3. All the data was placed in the data table.
4. The ways of the study could have been improved, investigated and described.

## Conclusion:

In this experiment, Kirchoff's Voltage Law (KVL) and Kirchoff's Current Law (KCL) was checked and verified both calculating and measuring, so the experiment was successful.

## Reference:

1. Robert L. Boylestad, "Introductory Circuit Analysis", 10th Edition.
2. Introduction to Electrical Circuit Laboratory, Experiment - Lab Manual.