

AMERICAN INTERNATIONAL UNIVERSITY-BANGLADESH

408/1, Kuratoli, Khilkhet, Dhaka 1229, Bangladesh



Assignment Title: Analysis of RLC parallel circuit and verification of KCL in AC circuits.

Assignment No: 09

Date of Submission: December 04, 2022

Course Title: Introduction to Electrical Circuits Laboratory

Course Code: COE2102

Section:

T

Semester: FALL

2022-23

Course Teacher: BISHWAJIT BANIK PATHIK

Declaration and Statement of Authorship:

1. I/we hold a copy of this Assignment/Case-Study, which can be produced if the original is lost/damaged.
2. This Assignment/Case-Study is my/our original work and no part of it has been copied from any other student's work or from any other source except where acknowledgement is made.
3. No part of this Assignment/Case-Study has been written for me/us by any other person except where such collaboration has been authorized by the concerned teacher and is clearly acknowledged in the assignment.
4. I/we have not previously submitted or currently submitting this work for any other course/unit.
5. This work may be reproduced, communicated, compared and archived for the purpose of detecting plagiarism.
6. I/we give permission for a copy of my/our marked work to be retained by the Faculty for review and comparison, including review by external examiners.
7. I/we understand that Plagiarism is the presentation of the work, idea or creation of another person as though it is your own. It is a form of cheating and is a very serious academic offence that may lead to expulsion from the University. Plagiarized material can be drawn from, and presented in, written, graphic and visual form, including electronic data, and oral presentations. Plagiarism occurs when the origin of the material used is not appropriately cited.
8. I/we also understand that enabling plagiarism is the act of assisting or allowing another person to plagiarize or to copy my/our work.

* Student(s) must complete all details except the faculty use part.

** Please submit all assignments to your course teacher or the office of the concerned teacher.

21

Group Name/No.: 8 / Ground

No	Name	ID	Program	Signature
1	MD. SHOHANUR RAHMAN SHOHAN	22-46013-1	B. Sc. in CSE	Shohan
2	MAHNAZ TABASSUM ORPITA	22-46024-1	B. Sc. in CSE	Oripita
3	LIDA KHAN MUKTI	22-47000-1	B. Sc. in CSE	Lida
4	TARIN SULTANA	22-47045-1	B. Sc. in CSE	Tarin
5	A. F. M. RAFIUL HASSAN	22-47048-1	B. Sc. in CSE	Rafiq

Faculty use only

FACULTY COMMENTS

Marks Obtained

21

Total Marks

Abstract:

The experiment was conducted to analyze of RLC circuit and verified KCL in AC circuit. The objective of this experiment are to determine phase relationship between I_L and R_C in a RLC parallel circuit and verify the KCL in AC circuits. In this experiment, some basic tools like oscilloscope, function generator, resistor, inductor, capacitor, connecting wire, multimeter, bread board etc are used. By completing this experiment, we can develop the understanding of RLC circuit and verified KCL.

Theory:

The definition of conductance (G) in dc circuit was $1/R$. The conductance of each branch was then added to determine the overall conductance of a parallel circuit. Simply said, R_T is equal to $1/G_T$. We define admittance (Y) in ac circuit as being equal to $1/Z$. According to the SI system, the unit of measurement for admission is the siemens, which is represented by the letter

As P

S. A measure of an ac circuit's ability to allow or permit current to flow, is called admittance. Therefore, for a given applied potential, a heavier circuit flow results from a bigger value. finding the sum of the parallel admittances is another method for determining the circuit's total admittance. The total impedance Z_T of the circuit is then $1/Y_T$; that is, for the network of fig-1.

$$Y_T = Y_1 + Y_2 + Y_3 + \dots + Y_N$$

$$\text{since } Z = 1/Y$$

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots + \frac{1}{Z_N}$$

for two impedances in parallel,

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$Z_T = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

for three parallel impedances,

$$Z_T = \frac{Z_1 Z_2 Z_3}{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}$$

As pointed out in the introduction to this section, conductance is the reciprocal of resistance, and

$$Y_R = \frac{1}{Z_R} = \frac{1}{R \angle 0^\circ} = G \angle 0^\circ$$

the reciprocal of reactance ($1/x$) is called susceptance and is a measure of how susceptible an element is to the passage of current through it. Susceptance is also measured in siemens and is represented by the capital letter B .

for the inductor,

$$Y_L = \frac{1}{Z_L} = \frac{1}{X_L \angle 90^\circ} = \frac{1}{X_L} \angle -90^\circ$$

$$B_L = \frac{1}{X_L} \text{ (siemens, S)}$$

$$Y_L = B_L \angle -90^\circ$$

Note that for inductance, an increase in frequency or inductance will result in a decrease in susceptance or, correspondingly, in admittance.

for the capacitor,

$$Y_C = \frac{1}{Z_C} = \frac{1}{X_C \angle -90^\circ} = \frac{1}{X_C} \angle 90^\circ$$



$$B_C = \frac{1}{X_C} \text{ (siemens, S)}$$

for the capacitor, therefore, an increase in frequency or capacitance will result in an

APP
• 0

increase in susceptance or, correspondingly, in admittance. for any configuration (series, parallel, serial, parallel, etc.), the angle associated with the total admittance is the angle by which the source current leads the applied voltage. for inductive networks, θ_T is negative, whereas for capacitive networks, θ_T is positive.

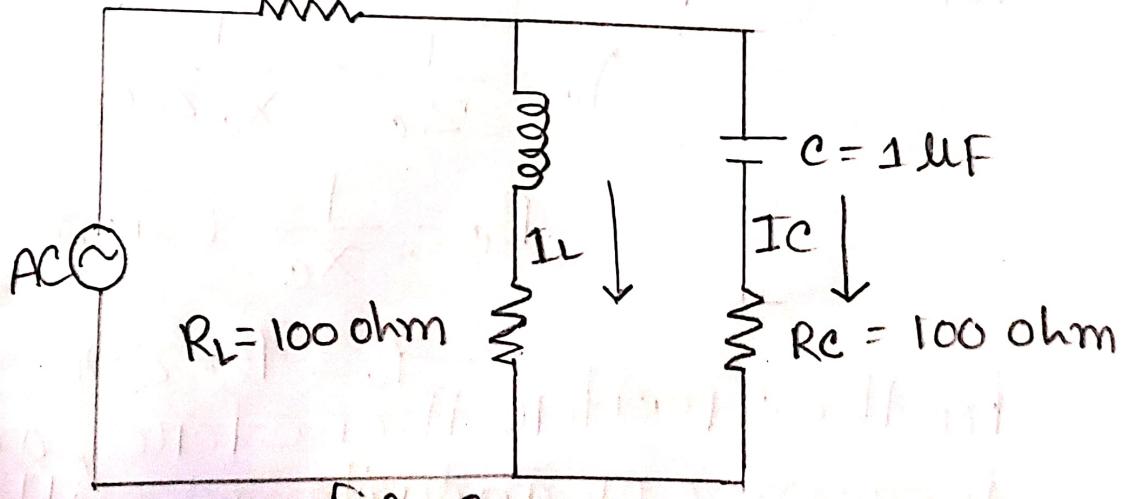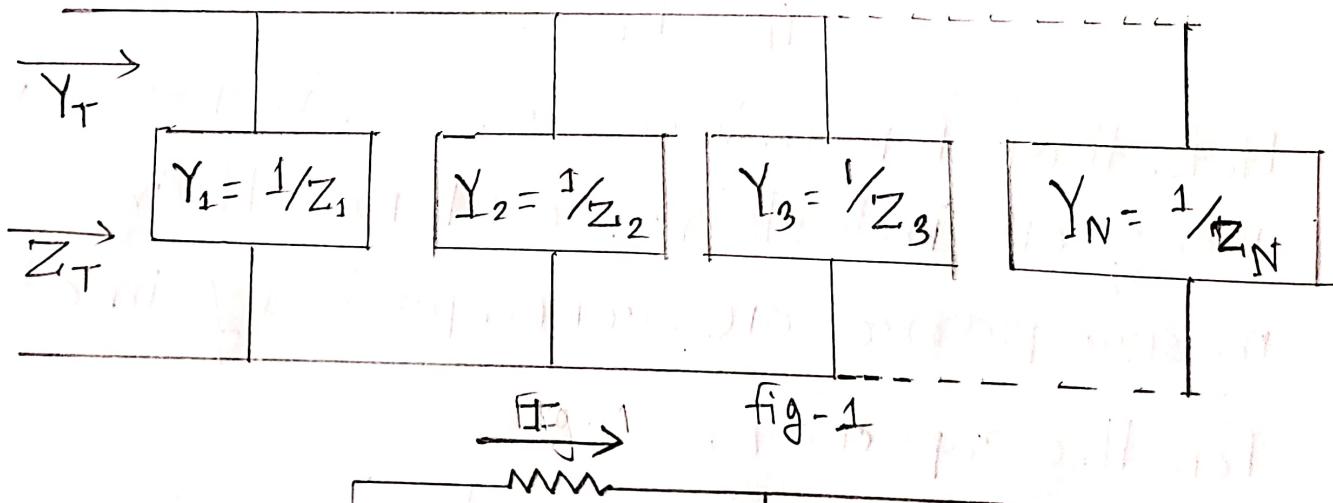the circuit of fig-2 represents a RLC parallel circuit where the total current I will divide into I_L and I_C in the parallel branches. If we apply KCL, $I = I_L + I_C$.



Apparatus :

- Oscilloscope
- Function generator
- Resistor
- Inductor
- Capacitor
- Connecting wire.
- Bread board.

precautions :

- proceed according to figure understanding the connections and check initially, if all the other buttons in the inductor and capacitor box are in off position or not.
- Operate the signal / function generator smoothly and connect the probes perfectly.
- Calibrate the oscilloscope before connecting the channels across any components to ensure that there is no problem in the probes of oscilloscope
- connect the components to the bread board smartly to ensure the connections .

Data Table:

f	F	V_{RL} volts	$I_L = V_{RL}/R_L$ A	θ_L	V_{RC} volts	$I_C = V_{RC}/R_C$	θ_C	$I_L + I_C$ A	V_R volts	$I = V_R/R$ A
1KHz	2	$414 \text{ mV} \times 0.707$	2.93	54°	$410 \text{ mV} \times 0.707$	2.92	58.5°	5.85	920×0.707	6.54
5KHz	2	$444 \text{ mV} \times 0.707$	0.99	63.45°	400×0.707	2.85	17.1°	3.84	444×0.707	3.15
10KHz	2	140×0.707	0.99	5.85°	500×0.707	3.56	85.5°	4.55	500×0.707	3.56

Calculations:-

① For 1 KHz:

$$f = 1 \text{ KHz}$$

$$\begin{aligned} V_R &= (920 \times 0.707) \text{ mV} \\ &= 651.854 \text{ mV} = 0.65 \text{ V} \end{aligned}$$

$$I_S = \frac{920 \times 0.707}{99.6}$$

$$= 6.54 \text{ mA}$$

$$\begin{aligned} V_{RL} &= 414 \text{ mV} \times 0.707 \\ &= 0.41 \text{ V} \times 0.707 \end{aligned}$$

$$I_{RL} = \frac{1.99}{99.1} = 2.93 \text{ mA}$$

$$\begin{aligned} V_{RC} &= 410 \text{ mV} \times 0.707 \\ &= 289.87 \text{ mV} \end{aligned}$$

$$I_{RC} = \frac{289.87}{99.4} = 2.92 \text{ mA}$$

$$I_s = 6.54 \text{ mA}$$

$$I_{RL} + I_{RC} = 5.85 \text{ mA}$$

L

$$T = 8 \times 500 \mu\text{s}$$

$$dt = 1.2 \times 500 \mu\text{s}$$

$$\begin{aligned}\theta_L &= \frac{dt \times 360^\circ}{T} \\ &= \frac{1.2 \times 500 \times 360^\circ}{8 \times 500} \\ &= 54^\circ\end{aligned}$$

C

$$T = 8 \times 500 \mu\text{s}$$

$$dt = 1.3 \times 500 \mu\text{s}$$

$$\begin{aligned}\theta_C &= \frac{1.3 \times 360^\circ}{8} \\ &= 58.5^\circ\end{aligned}$$

② For L 5 kHz

$$f = 5 \text{ kHz}$$

$$V_R = 444 \times 0.707 \text{ mV}$$

$$\begin{aligned}I_R &= \frac{444 \times 0.707}{99.6} \\ &= 3.15 \text{ mA}\end{aligned}$$

$$V_{RL} = 140 \times 0.707 \text{ mV}$$

$$I_{RL} = \frac{140 \times 0.707}{99.1} = 0.99 \text{ mA}$$

$$V_{RC} = 400 \text{ mV} \times 0.707$$

$$I_{RC} = \frac{400 \times 0.707}{99.4}$$

$$= 2.85 \text{ mA}$$

$$I_R = 3.15 \text{ mA}$$

$$I_{RC} + I_{RL} = 3.84 \text{ mA}$$

$$\underline{\theta_L} \quad T = 8 \times 100 \mu\text{s}$$

$$t_d = 1.41 \times 100 \mu\text{s}$$

$$\underline{\theta_L} = \frac{1.41 \times 360}{8}$$

$$= 63.45^\circ$$

$$\underline{\theta_C} \quad L_d = 0.38 \times 100 \mu\text{s}$$

$$\underline{\theta_C} = \frac{0.38 \times 360}{8}$$

$$= 17.1^\circ$$

③ For 10 kHz

$$f = 10 \text{ kHz}$$

$$V_{RC} = 500 \text{ mV} \times 0.707$$

$$I_{RC} = \frac{500 \times 0.707}{99.1}$$

$$= 3.56 \text{ mA}$$

$$V_{RL} = 140 \text{ mV} \times 0.707$$

$$I_{RL} = \frac{140 \times 0.707}{99.1} = 0.99 \text{ mA}$$

$$V_R = 820 \text{ mV} \times 0.707$$

$$I_R = \frac{820 \times 0.707}{99.6}$$
$$= 5.82 \text{ mA}$$

$$I_R = 5.82 \text{ mA}$$

$$I_{RL} + I_{RC} = 1.55 \text{ mA}$$

$$\underline{Q_C} \quad T = 8 \times 50 \mu\text{s}$$

$$T_d = 0.13 \times 50 \mu\text{s}$$

$$\theta_C = \frac{0.13 \times 360^\circ}{8}$$
$$= 5.85^\circ$$

$$\underline{Q_L} \quad t_d = 1.9 \times 50 \mu\text{s}$$

$$\theta_L = \frac{1.9 \times 360^\circ}{8}$$
$$= 85.5^\circ$$

Theoretically :

① For, 1 kHz

$$X_L = 2\pi f L$$

$$= 2 \times 3.1416 \times 1000 \times 20 \times 10^{-3}$$

$$= 125.664 \Omega$$

$$X_C = \frac{1}{2\pi f C}$$

$$= \frac{1}{2 \times 3.1416 \times 1000 \times 10^{-6}}$$

$$= 159.15 \Omega$$

(b) + ✓

$$Z_s = 100 \Omega$$

$$Z_C = (100 - j125.67)$$

$$Z_L = (100 + j125.664) \Omega$$

$$Z_{LC} = \frac{Z_L Z_C}{Z_L + Z_C}$$

$$= 50.01 - 62.83j$$

$$Z_T = Z_C + Z_{LC}$$

$$= 150.01 - 62.83j$$

$$I_S = \frac{E}{Z_T}$$

$$= \frac{2}{150.01 - 62.83j}$$

$$= 0.01 + 4.75 \times 10^3 A$$

$$V_{LC} = \frac{Z_{LC}}{Z_T} E$$

$$= 6.865 - 0.475j$$

$$I_L = \frac{V_{LC}}{R_C}$$

$$= \frac{0.865 - 0.475}{100} = 8.65 \times 10^{-3} - 4.75 \times 10^{-3} j$$

$$I_C = \frac{V_{LC}}{R_C}$$

$$= 8.65 \times 10^{-3} - 4.75 \times 10^{-3} j$$

② For 5kHz

$$X_L = 2\pi f L$$

$$= 2 \times 3.1416 \times 5000 \times 20 \times 10^{-3}$$

$$= 628.32 \Omega$$

$$X_C = \frac{1}{2\pi f C}$$

$$= \frac{1}{2 \times 3.1416 \times 1000 \times 10^{-6}}$$

$$= 31.83 \Omega$$

$$Z_s = 100 \Omega$$

$$Z_C = 100$$

$$Z_{LC} = \frac{Z_L Z_C}{Z_L + Z_C}$$

$$= 105.68 - 30.81j$$

$$Z_T = Z_R + Z_{LC}$$

$$= 205.68 - 30.80j$$

$$I = \frac{E}{Z_T}$$

$$= \frac{2}{205.68 - 30.80j}$$

$$= 9.51 \times 10^{-3} + 1.42 \times 10^{-3}$$

$$V_{LC} = \frac{Z_{LC}}{Z_T} \times E$$

$$= 1.04 - 0.14j$$

$$I_L = \frac{V_{LC}}{R_L}$$

$$= \frac{1.04 - 0.14j}{100}$$

$$= 0.011 - 1.43j$$

$$I_C = \frac{V_{LC}}{R_C}$$

$$= \frac{1.04 - 0.14j}{100}$$

$$= 0.011 - 0.143j$$

③ For 10 kHz

$$X_L = 2\pi f L$$

$$= 2 \times 3.1416 \times 10000 \times 20 \times 10^{-3}$$

$$= 1256.64 \Omega$$

$$X_C = \frac{1}{2\pi f C}$$

$$= \frac{1}{2 \times 3.1416 \times 1000 \times 10^{-6}}$$

$$= 0.0159 \Omega$$

$$Z_R = 100 \Omega$$

$$Z_C = 100 - 0.0159j$$

$$Z_L = 100 + 1256.64j$$

$$Z_{LC} = \frac{Z_L Z_C}{Z_L + Z_C}$$

$$= 0.0159 + 7.74j$$

$$Z_T = Z_R + Z_{LC}$$

$$= 100 + 0.0159 + 0.0159 + 7.74j$$

$$I = \frac{E}{Z_T}$$

$$= \frac{2}{100 + 0.0159 + 0.0159 + 7.74j}$$

$$= 0.01 - 3.9 \times 10^{-4}j$$

$$V_{LC} = \frac{Z_{LC}}{Z_T} \times E$$

$$= 0.995 \times 0.039j$$

$$I_L = \frac{V_{LC}}{R_L}$$

$$= \frac{0.995 + 0.039j}{100}$$

$$= 9.95 \times 10^{-3} + 3 \times 10^{-4}j$$

$$I_C = 9.95 \times 10^{-3} + 3 \times 10^{-4}j$$

Result :

from the data table

for 1 KHz,

$$I_L + I_C = 5.85 \text{ mA}$$

$$I_S = 6.54 \text{ mA}$$

$$I_L + I_C \approx I_S$$

for 5 KHz,

$$I_L + I_C = 3.84 \text{ mA}$$

$$I_S = 3.15 \text{ mA}$$

$$I_L + I_C \approx I_S$$

for 10 KHz,

$$I_L + I_C = 54.55 \text{ mA}$$

$$I_S = 3.56 \text{ mA}$$

$$I_L + I_C \approx I_S$$

for all the frequency $I_L + I_C$ is almost close to I_S

Discussion:

In this experiment, first of all we checked the Oscilloscope and if the probs were perfect we started calibration. Then we converted to the prob to the channel. In function generator and also right frequency in there. After doing all these things we got a value which was very close to our expected value.

Conclusion:

In this experiment we have analyzed RLC parallel circuit and verified KCL in AC circuit. This was the summation of I_L & I_C is almost equal to the I_S . so the, Σ entering current = Σ leaving current. The experiment was conducted successfully.

References:

1. R.M Kerchhenerz and Gr.F. concorn, "Alternating current circuits"; John wiles & sons. Third Ed, New York., 1956.