

i 1) Outline for designing the alarm circuit:-

Steps:-

- ① Analyzing the problem - statement
- ② Finding the inputs and outputs of the system
- ③ Relating the inputs and outputs.
- ④ Creating the truth table.
- ⑤ Forming a standard expression from the truth table.
- ⑥ Simplifying the expression using K-MAP.
- ⑦ Designing the system circuit by logic gates.
- ⑧ Implementing the system with CMOS logic.

Step-1:-

There are four sensors in a car. The ignition activation system of this car is attached to a digital system. If the driver's seat is occupied and the driver's seatbelt is fastened on the passenger seat is occupied and the passenger's seatbelt is fastened, then the activation system turns on. There are appropriate sensors present for detecting the above.

Step-2:-

There are appropriate sensors present for detecting the activation, which are the inputs of the system.

→ Where,

A = sensor for driver seat.

B = sensor for driver seatbelt.

C = sensor for passenger seat.

D = sensor for passenger seatbelt.

An output Y will be generated for given conditions.

Step-3:-

when A and B is high on A and B and C also D is high, the output will be high otherwise the output will be low.

Step-4:-

	A	B	C	D	Y
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

Step-5:-

$$Y = \Sigma (12, 13, 14, 15)$$

$$= AB\bar{C}\bar{D} + AB\bar{C}D + ABC\bar{D} + ABCD$$


Step-6:-

0	1	2	3
4	5	6	7
8	9	10	11
12	13	14	15

A	B	C	D
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1
A	B	X	X

$$\therefore Y = AB$$


Step-7:-

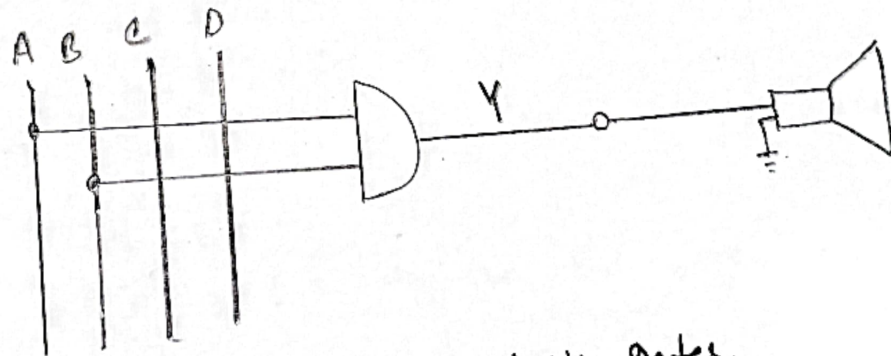

Design of the system using basic gates.

Here, when both A and B sensor inputs are high (1), then the output of the system will be high and the alarm speaker will get enough voltage to make on create a sound. Thus, in this way the alarm can be triggered.

Step-8:-

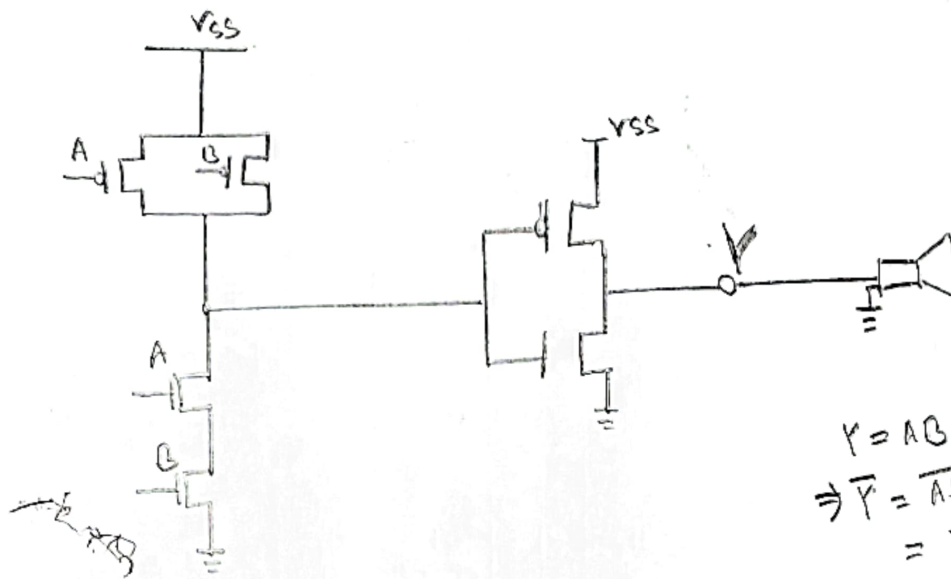

$$Y = AB$$

$$\Rightarrow \bar{Y} = \overline{AB} \rightarrow \text{NMOS}$$

$$= \bar{A} + \bar{B} \rightarrow \text{PMOS}$$

Implementation of the system using CMOS logic.

ii

ii) Given,

$$P = N + O + I + S + E$$

$$= 4 + 7 + 0 + 4 + 8$$

$$= 23$$

$$\therefore P * 20 \text{ Hz} = 23 * 20$$

$$= 460 \text{ Hz} \text{ [within the soothing hearing limits]}$$

$$\therefore \text{frequency, } f = 400 \text{ Hz}$$

Hence,

$$\theta = 100 - P$$


$$= 100 - 23$$

$$= 77$$

$$\therefore \text{Duty cycle, } \theta = \cancel{77} \rightarrow 77\%$$

$$\therefore \theta = 77\%$$

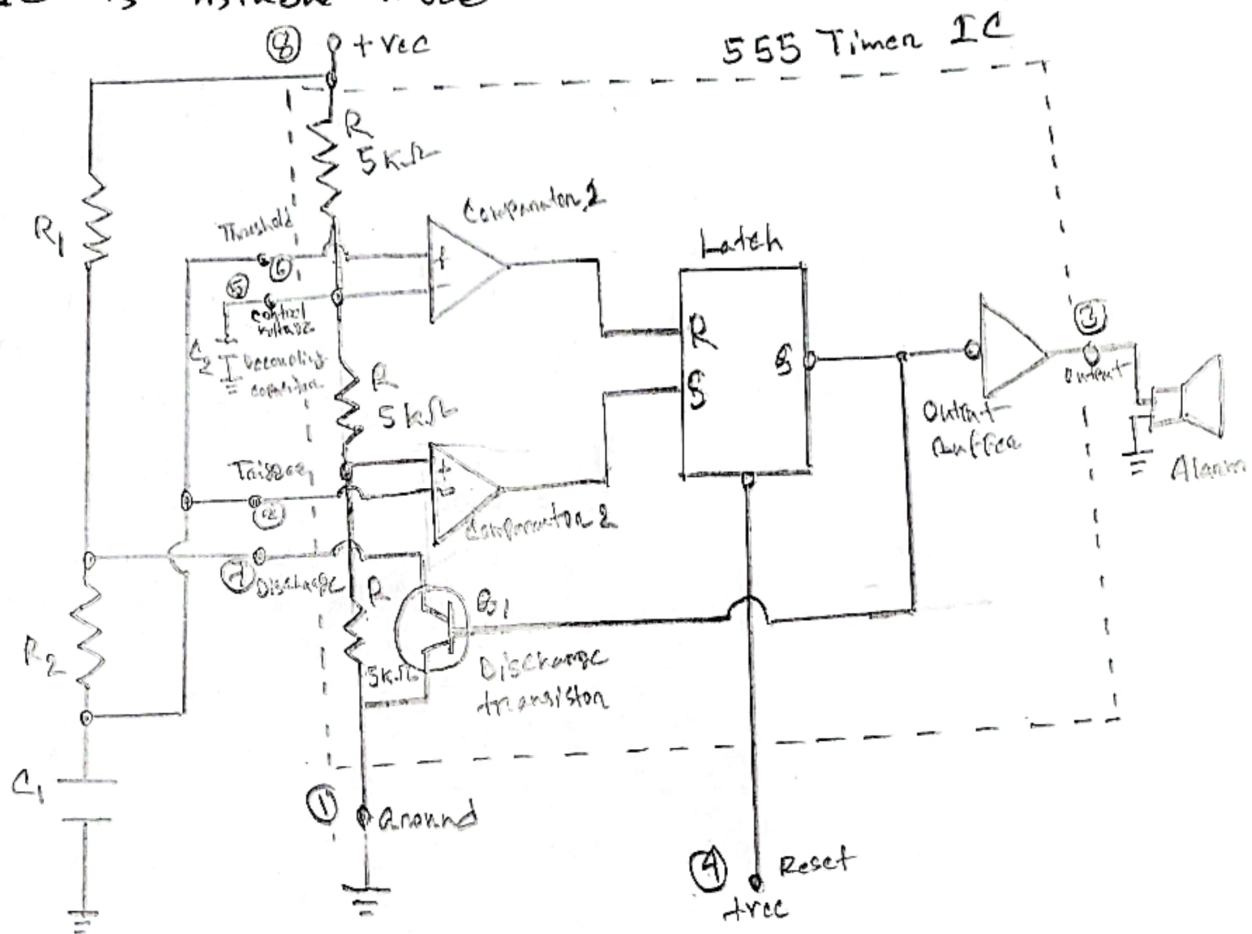→ Now, we can design the alarm timer circuit with 555 timer IC in Astable mode.



Here,
400Hz is not a very high frequency, so, we need a 250µF (C1)
and a 50µF (C2) as decoupling capacitor.

So, Time Period, $T = \frac{1}{f} = \frac{1}{400} = 0.0025s$

We know,

Duty cycle, $\phi = \frac{T_H}{T}$

$\Rightarrow T_H = \phi \times T = 0.77 \times 0.0025$
 $= 0.001925s$

$T_L = T - T_H = 0.0025 - 0.001925$
 $= 0.000575s$



And, $T_L = 0.693 R_2 C_1$

$\Rightarrow R_2 = \frac{T_L}{0.693 \times C_1} = \frac{0.000575}{0.693 \times 250 \times 10^{-6}}$
 $= 3.463 \Omega$

Now, $T = 0.693 C_1 (R_1 + 2R_2)$

$\Rightarrow R_1 = \frac{T}{0.693 \times C_1} - 2R_2$
 $= \frac{0.0025}{0.693 \times 250 \times 10^{-6}} - (2 \times 3.463) = 7.504 \Omega$

Final Circuit diagram with values:-

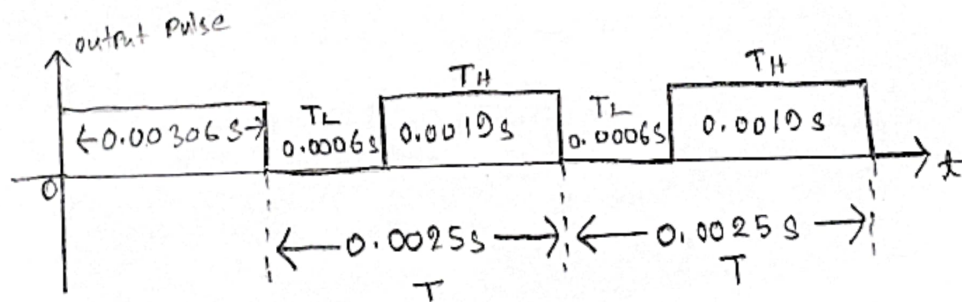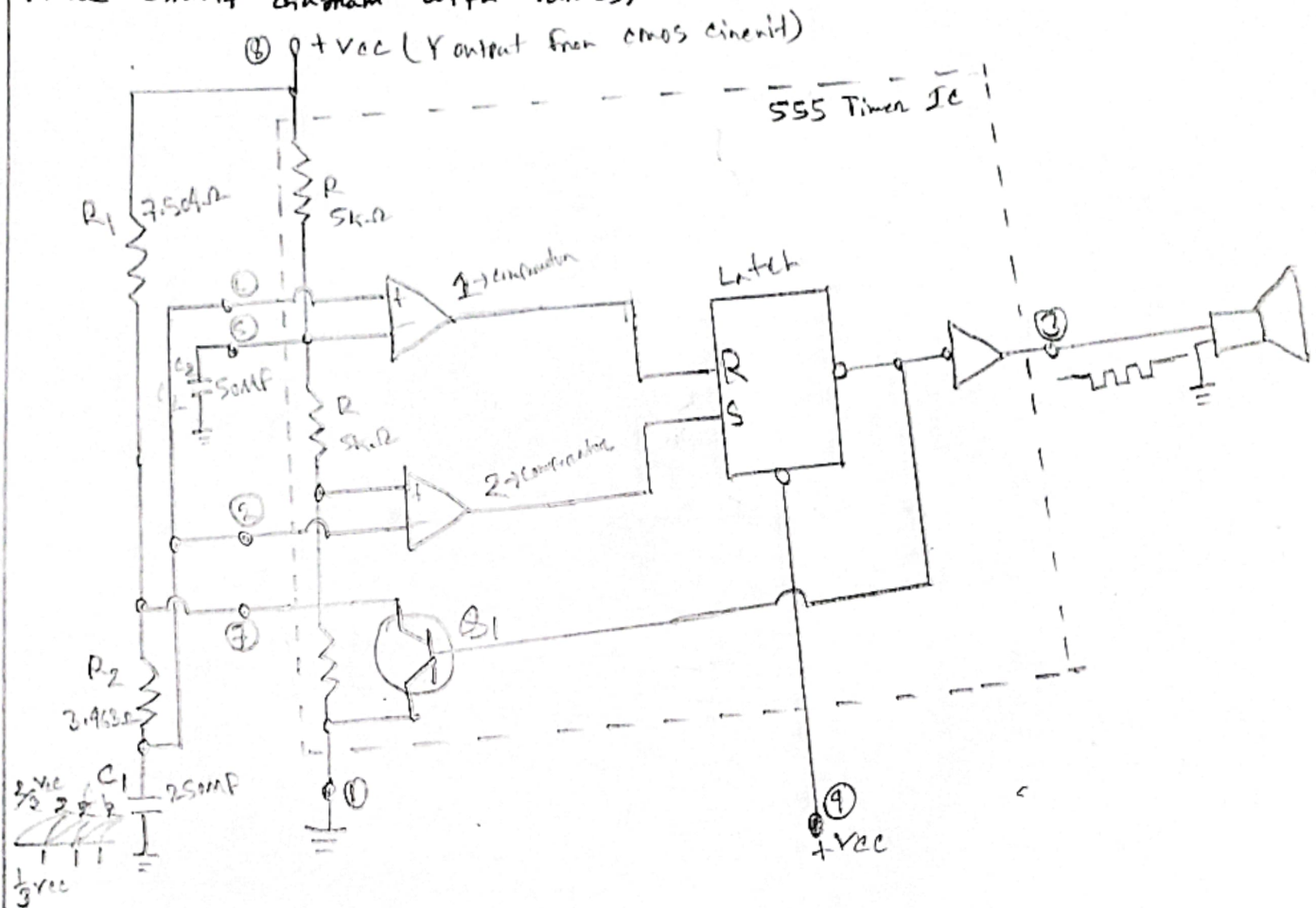

Initially, the capacitor takes 0.00306s to charge from 0 - $\frac{2}{3} V_{cc}$.

So, we get output time period of 0.0025s after the initial 0.00306s. That's why the alarm will be buzz for 0.0019s and stop for 0.0006s and it will maintain the frequency which is 400 Hz.

iii
iii) Limitations:-

- ① The system heavily relies on accuracy and reliability of sensors. Any inaccuracies in these sensors can lead to false readings and incorrect activation of ignition.
- ② It may generate false alarms if sensors detect incorrect information.
- ③ It's functionality is limited to detecting driver and passenger seat occupancy and seatbelt status. It does not account for other factors that could influence safe driving condition, such as the condition of the driver, vehicle speed or road conditions.
- ④ Any failure in the car's electrical system, such as a dead battery or other component failure could affect the function of the system.

Effect of increasing frequency above 4500 Hz:-

- ① Frequencies above 4500 Hz are considered disturbingly high-pitched. Increasing the alarm frequency beyond this limit could lead to discomfort, unpleasant or even potential harm to individual's hearing.
- ② At higher frequency, problem can be occur with the.

555 Timer IC.